

DIGITAL SYSTEM

PRACTICUM REPORT 4 : LOGIC GATE COMBINATION



NIM : L200184172

NAME : HAFSHAH FITRI AFIFAH

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS


MUHAMMADIYAH UNIVERSITY OF SURAKARTA

2019

NIM : L200184172
NAME : HAFSHAH FITRI AFIFAH
CLASS : X
ASSISTANT : SALSA SASMITA MUKTI
DATE OF PRACTICUM : Friday, March 22th 2019

#ADDITIONAL ASSIGNMENT

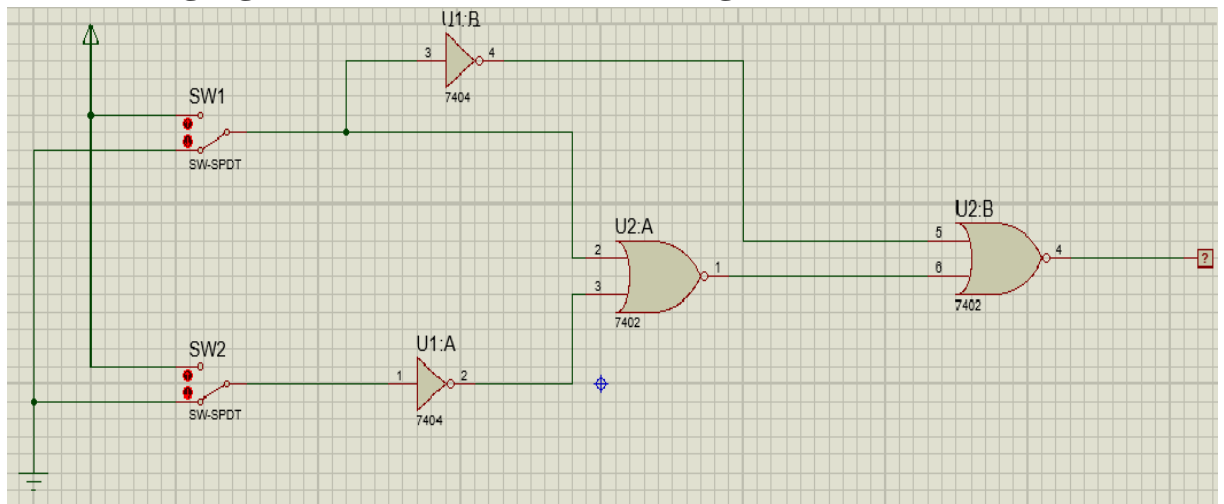1. Create a logic gate combination as show in figure below!




a) Truth table

X	Y	L ₁
0	0	0
1	0	1
0	1	0
1	1	1

b) Time diagram



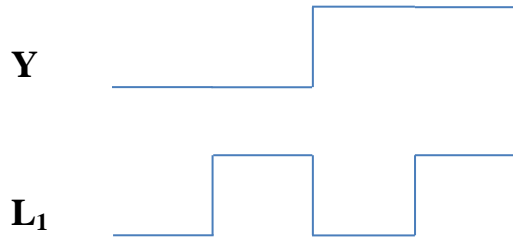

c) Boolean function

$$\overline{(\overline{X + Y}) + \overline{X}}$$

2. Create a logic gate circuit based on the following Boolean function!

$$F = (\overline{A} \cdot \overline{B} + C) + (\overline{D} \cdot E)$$

